

COMP1071 - Digital Electronics

Circuits

Ioannis Ivrissimtzis

email: ioannis.ivrissimtzis@durham.ac.uk

Room: MCS 2023

Slide acknowledgements: Eleni Akrida and Farshad Arvin

Overview of today's lecture

- Adder
- Subtractor
- Decoder
- Tristates
- Mux
- Simple ALU

Key circuits

Combinatorial / combinational circuits:

(Output depends only on current input)

Adders – add the contents of two registers

Decoders – decodes an n-digit binary number into 2^n data lines

Multiplexors – use a binary number to select an input

Sequential circuits

(Output depends on state and input, i.e. history of input)

Latches / flip-flops – basic memory element

Half-Adder

Based on 8 simple rules:

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 0 \text{ with Carry}$$

$$\text{Carry} + 0 + 0 = 1$$

$$\text{Carry} + 0 + 1 = 0 \text{ with Carry}$$


$$\text{Carry} + 1 + 0 = 0 \text{ with Carry}$$

$$\text{Carry} + 1 + 1 = 1 \text{ with Carry}$$

Inputs: A, B

Outputs: Sum, Carry


A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

Adder


Input is not just A and B, but A, B and **the carry from the previous bit**

 Use two half-adders: Add A and B first, then add in the carried bit:



Chaining adders – ripple carry adder

How to add two 4 bit registers:

 


More full-adders can be chained together to give 8-, 16- or 32-bit adders.

Subtractor

Recall that we can create a **twos-complement negative** by inverting each bit and adding 1.

 We subtract b from a by **adding $-b$** .



The NOT gates and setting $C_{in}=1$ give the effect of converting b to $-b$.

Beyond Simple Logic Gates - Decoder


A decoder has N inputs and 2^N outputs. Asserts exactly one of its outputs depending on the binary number represented by the N input bits.

The outputs are called *one-hot*, because exactly one is “hot” (high) at a given time.

N inputs, **2^N** outputs.


Only one output is high at a time.

Which one depends on the input.

 


Decoder

2-bit decoder:

 

Unique 1
in each
row

A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

 


Decoder

Larger decoders require multi-input AND gates to be constructed.

This requires a lot of circuitry.

Can create deeper circuits with fewer transistors (i.e. less silicone), at the cost of slower response.

3-bit or '3-8' decoder

 


Beyond Simple Logic Gates - Mux (multiplexor)

Chooses 1 of many inputs to steer to its single output under the direction of control inputs (selector)

e.g., if the input to a circuit can come from several places a Mux is one way to funnel the multiple sources selectively to the single input.

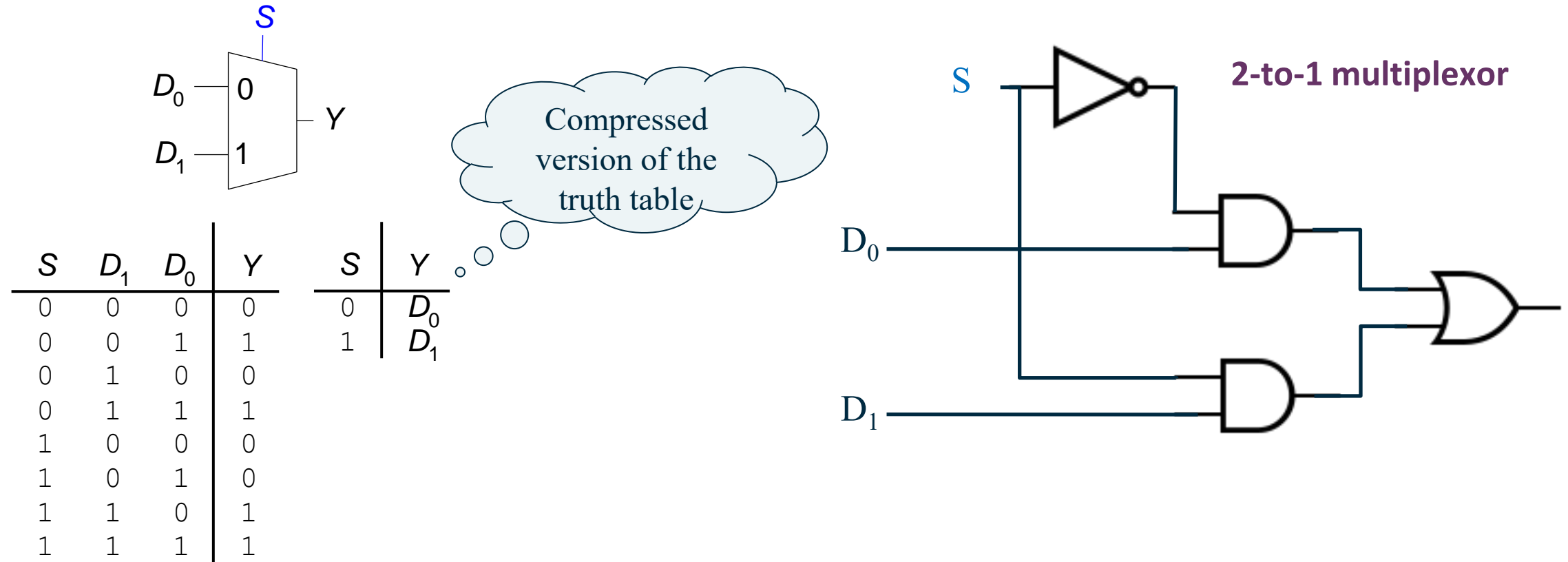Beyond Simple Logic Gates - Mux (multiplexor)



A multiplexor has **$k+2^k$ inputs** and **1 output**.

The first k inputs (the selector S) represent a binary number.



The output takes the value of one of the remaining **2^k inputs**, the one indexed by the selector.

Overview of today's lecture

- Adder
- Subtractor
- Decoder
- Tristates
- Mux
- Simple ALU

Tristate

  
In contrast to a normal **buffer** which is either 1 or 0 at its output, a tristate buffer can be electrically disconnected from the bus wire, i.e., it will have no effect on any other signals currently on the bus.




A single transistor could work, but the output is not driven.

Input	Enable	Output
0	0	Floating
0	1	0
1	0	Floating
1	1	1

Linear truth table

 


Inverting Tristate

 



Input	Enable	Output
0	0	Floating
0	1	1
1	0	Floating
1	1	0

Linear truth table

 

Here the output is driven by direct connection to VDD or ground.


Tristate

  

Input	Enable	Output
0	0	Floating
0	1	0
1	0	Floating
1	1	1


Linear truth table

Mux (multiplexor)

 

S	D_1	D_0	Y	S	Y
0	0	0	0	0	D_0
0	0	1	1	1	D_1
0	1	0	0		
0	1	1	1		
1	0	0	0		
1	0	1	0		
1	1	0	1		
1	1	1	1		



2-to-1 line multiplexor

 

It looks like Y is driven by two outputs which violates the combinational circuit rules, but this is not in fact the case; we have been very careful in how the selectors are arranged so that only one of T_0, T_1 is ever driving the value, and the other is floating.

Mux

4-to-1 line multiplexor

  


(a)

- a) **two-level logic**, requiring multiple input gates.
- b) Using **tri-state** buffers – take value of input if activated, otherwise floating value.
- c) Using **hierarchical logic**

Mux (example 2.12 in Harris & Harris)

- A Mux can be used to implement combinational logic functions.
- An 8-input Mux can be used to implement functions in three variables. For example:

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

 

The control inputs A, B, C are used to select the minterms required at the output.


Mux (example 2.13 in Harris & Harris)

More economic designs than the one in the previous slide are possible.



For example, reduce the truth table to 4 rows by letting the output depend on C.

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

A	B	Y
0	0	\bar{C}
0	1	C
1	0	1
1	1	0

 

 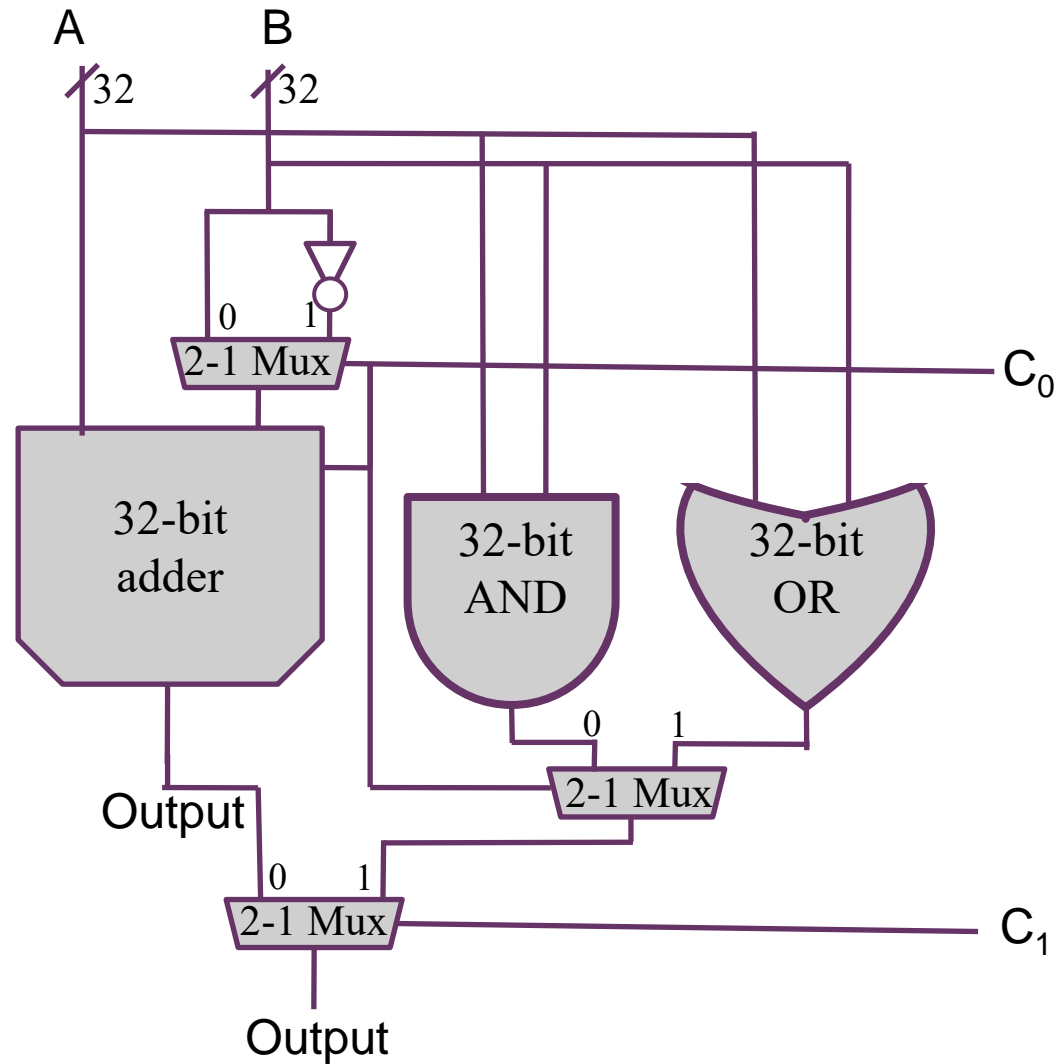Building a simple ALU (Arithmetic Logic Unit)



C_0
0
1

F_n
Add
Subtract

Summary

- Adder & Subtractor
- Decoder & Mux
- Tristates
- ALU