

# **COMP1071 - Digital Electronics**

## **Transistors and Logic Gates**

**Ioannis Ivrissimtzis**

**email:** [ioannis.ivrissimtzis@durham.ac.uk](mailto:ioannis.ivrissimtzis@durham.ac.uk)

**Room:** MCS 2023

**Slide acknowledgements:** Eleni Akrida and Farshad Arvin

# Overview of today's lecture

- Transistors
- Logic gates and truth tables
- Logic Levels
- Moore's Law

# Transistors

Babbage's Analytical Engine – gears

Early electrical computers – relays or vacuum tubes


Modern computers – **transistors!**

Electrically controlled switches that turn ON or OFF when voltage or current is applied to a control terminal.

Most common transistor is the MOSFET:

 
**Metal-Oxide-Semiconductor Field Effect Transistor.**

- 57 billion MOSFETs onto a single chip of silicon!
- Building blocks of almost all digital systems.





 
# From Transistors to Digital circuits

- Digital Circuits are constructed from small electronic circuits called **logic gates**
  - Each logic gate is designed to perform a function of **Boolean logic**
  - A logic gate is created from one or more **transistors**
    - The output of a logic gate can feed into more logic gates...


   
# Transistors

- 2 ports (d and s) are connected depending on voltage of 3<sup>rd</sup> (g)



# Adding in binary

Example

$\begin{array}{r} 11100 \\ +01110 \\ \hline \end{array}$	$\begin{array}{r} 11100 \\ +01110 \\ \hline 0 \end{array}$	$\begin{array}{r} 11100 \\ +01110 \\ \hline 10 \end{array}$	$\begin{array}{r} 1 \\ 11100 \\ +01110 \\ \hline 010 \end{array}$	$\begin{array}{r} 11 \\ 11100 \\ +01110 \\ \hline 1010 \end{array}$	$\begin{array}{r} 111 \\ 11100 \\ +01110 \\ \hline 01010 \end{array}$	$\begin{array}{r} 111 \\ 11100 \\ +01110 \\ \hline 101010 \end{array}$
--	--	---	---	---	---	--

Based on 8 simple rules:

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 0 \text{ with Carry}$$

$$\text{Carry} + 0 + 0 = 1$$



$$\text{Carry} + 0 + 1 = 0 \text{ with Carry}$$

$$\text{Carry} + 1 + 0 = 0 \text{ with Carry}$$

$$\text{Carry} + 1 + 1 = 1 \text{ with Carry}$$
  
# How is this achieved?

- Using **gates** implementing **Boolean algebra**.
- **Boolean algebra:**  
an algebra of two values: **1,0**  
or **True/False** or **high/low voltage**.
- Basic operations: AND, OR, NOT
  - $0 \text{ AND } 0 = 0$
  - $0 \text{ AND } 1 = 0$
  - $1 \text{ AND } 0 = 0$
  - $1 \text{ AND } 1 = 1$



# Truth tables: AND

- **AND** gate:  Algebraic expression:  $Y = A \cdot B$

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

Linear truth table

AND	0 <sup>B</sup>	1
0 <sup>A</sup>	0	0
1	0	1

Rectangular/Coordinate table



# Truth tables: OR

- **OR** gate:  Algebraic expression:  $Y = A + B$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

Linear truth table

OR	0 <sup>B</sup>	1
0 <sup>A</sup>	0	1
1	1	1

Rectangular/Coordinate table

# Truth tables: Exclusive OR (XOR)

- XOR** gate:  Algebraic expression:  $Y = A \oplus B$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

Linear truth table

AND		B	
		0	1
A	0	0	1
	1	1	0

Rectangular/Coordinate table

# Truth tables: NOT

- NOT** gate:  Algebraic expression:  $Y = \bar{A}$

A	Y
0	1
1	0

Linear truth table


# Truth tables: NOR

- **NOR** gate (inverse of OR)



Algebraic expression:  $Y = \overline{A + B}$


||

 


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

Linear truth table

# From transistors to gates

- A **NOT** gate: 
- If **A** is **high** then the p-MOS P1 is off and the n-MOS N1 is on, so **Y** is connected to GND, i.e. **low**.
- If **A** is **low** then the p-MOS P1 is on and the n-MOS N1 is off, so **Y** is connected to  $V_{DD}$ , i.e. **high**.


A	P1	N1	Y
0	on	off	1
1	off	on	0

 

# From transistors to gates

- A **NAND** gate: 

A	B	P1	P2	N1	N2	Y
0	0					
0	1					
1	0					
1	1					

 


**Note:** 3-wire junctions are connected, but 4-wire junctions are only connected if there is a dot.

# From transistors to gates

- A **NAND** gate: 


A	B	P1	P2	N1	N2	Y
0	0	on	on	off	off	1
0	1					
1	0					
1	1					

 

# From transistors to gates

- A **NAND** gate: 

A	B	P1	P2	N1	N2	Y
0	0	on	on	off	off	1
0	1	on	off	off	on	1
1	0					
1	1					

 




# From transistors to gates

- A **NAND** gate: 


A	B	P1	P2	N1	N2	Y
0	0	on	on	off	off	1
0	1	on	off	off	on	1
1	0	off	on	on	off	1
1	1					

 

# From transistors to gates

- A **NAND** gate: 


A	B	P1	P2	N1	N2	Y
0	0	on	on	off	off	1
0	1	on	off	off	on	1
1	0	off	on	on	off	1
1	1	off	off	on	on	0

 
 
# From transistors to gates

- An **AND** gate: 

Essentially made by combining a NAND and a NOT gate.





# Beneath the digital abstraction

A chip does not really deal in 0s and 1s.

The **voltages** are real numbers between 0V and 5V (typically).

We can take 0V to indicate output 0 and 5V to indicate output 1, but we need to tolerate **noise**.

  If the output is 4.9V that is probably meant to be a 1.  
But what about 4.1V or 3V or 2.5V?



# Supply voltage


The **low** voltage in the system (connected to **ground** or GND) is 0V.

Historically the circuit was powered by connecting to a 5V supply, and the **high** voltage is therefore 5V, called  $V_{DD}$  if unspecified.

More modern chips, using much smaller transistors, have moved to  $V_{DD} = 3.3V, 2.5V, 1.8V, 1.5V$  and  $1.2V$ , both to save power and avoid overloading transistors.

The mapping of the continuous voltage measured at any point in the circuit to the discrete 0 and 1 of the digital abstraction is governed by defining **logic levels**.

# Logic levels

 

Permitted range for high output:  $V_{OH}$  to  $V_{DD}$

Permitted range for low output: GND to  $V_{OL}$

Acceptable range for high input:  $V_{IH}$  to  $V_{DD}$

Acceptable range for low input: GND to  $V_{IL}$

Noise margins:

$$NM_H = V_{OH} - V_{IH}$$

$$NM_L = V_{IL} - V_{OL}$$

# The Static Discipline

- A guarantee that “if inputs meet **valid input thresholds**, then the system guarantees outputs will meet **valid output thresholds**” and will not fall into the forbidden zone
- Gates are grouped into **logic families**: the gates of the same family obey the static discipline when used with other gates in the family.
- This means that (given noise limits) you can successfully apply the **digital abstraction** and **combine elements** without further concern about logic levels or analogue values.

Logic Family	$V_{DD}$	$V_{IL}$	$V_{IH}$	$V_{OL}$	$V_{OH}$
TTL	5 (4.75 - 5.25)	0.8	2.0	0.4	2.4
CMOS	5 (4.5 - 6)	1.35	3.15	0.33	3.84
LVTTL	3.3 (3 - 3.6)	0.8	2.0	0.4	2.4
LVC MOS	3.3 (3 - 3.6)	0.9	1.8	0.36	2.7

# Moore's law

Gordon Moore co-founded Intel in 1968.

In 1965 he observed that the number of transistors on a computer chip doubles every year.

**Moore's law:** normally quoted as “transistor density doubles in 2 years”, or “computer processing power doubles every 18 months”.




# Moore's law

## Mastering Moore's Law

Intel's progress in packing more transistors on mainstream microprocessor chips


Logarithmic scale

 

\*Upgraded versions of prior models  
Source: Intel

THE WALL STREET JOURNAL.

# Moore's law

 

# transistors available for use by a 'domestic' computer.  
A lot of the growth recently has been in more powerful graphics cards available.

# Moore's law



“If the automobile had followed the same development cycle as the computer, a Rolls-Royce would today cost \$100, get one million miles to the gallon, and explode once a year . . .”

**Robert Cringely**



# Summary

- Transistors, pMOS & nMOS
- Logic gates and truth tables
- Logic Levels
- Moore's Law